

Name Index Number..... /

Powered By: www.manyamfranchise.com

232/3

PHYSICS
(PRACTICAL)

Candidate's Signature.....

Paper 3

Date.....

Oct./Nov. 2014

2½ hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL
Kenya Certificate of Secondary Education
PHYSICS
(PRACTICAL)
Paper 3
2½ hours

Instructions to candidates

- (a) Write your name and index number in the spaces provided above.
- (b) Sign and write the date of examination in the spaces provided above.
- (c) Answer **all** the questions in the spaces provided in the question paper.
- (d) You are supposed to spend the first 15 minutes of the 2½ hours allowed for this paper reading the whole paper carefully before commencing your work.
- (e) Marks are given for a clear record of the observations actually made, their suitability, accuracy and the use made of them.
- (f) Candidates are advised to record their observations as soon as they are made.
- (g) **Non-programmable** silent electronic calculators and KNEC mathematical tables may be used.
- (h) **This paper consists of 9 printed pages.**
- (i) **Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.**
- (j) **Candidates should answer the questions in English.**

For Examiner's Use Only

Question 1

	a	b	c	d	e	f	g	Total	
Maximum Score	2	1	2	5	4	2	4		
Candidate's Score									

Question 2

	d	e	f	g	Total	
Maximum Score	6	5	3	6		
Candidate's Score						

Grand Total	
--------------------	--

QUESTION 1

You are provided with the following:

- a voltmeter
- a milliammeter
- a micrometer screw gauge (to be shared)
- a stopwatch
- a centre zero galvanometer
- a switch
- ten connecting wires (at least five with a crocodile clip on one end)
- a resistance wire mounted on a millimetre scale labelled AB.
- a resistance wire labelled P.
- a resistance wire labelled Q.
- a capacitor labelled C.
- a metre rule or half metre rule.
- two dry cells and a cell holder.
- a carbon resistor labelled R.

Proceed as follows:

PART A

(a) Using the micrometer screw gauge provided, measure the diameter:

(i) D of wire P.

D = _____ (1 mark)

(ii) d of wire Q

d = _____ (1 mark)

(b) Determine C_1 the value of the ratio $\frac{D}{d}$.

$C_1 =$ _____ (1 mark)

- (c) (i) Set up the circuit as shown in **Figure 1**. (Ensure that each of the wires **P** and **Q** is 50cm long)

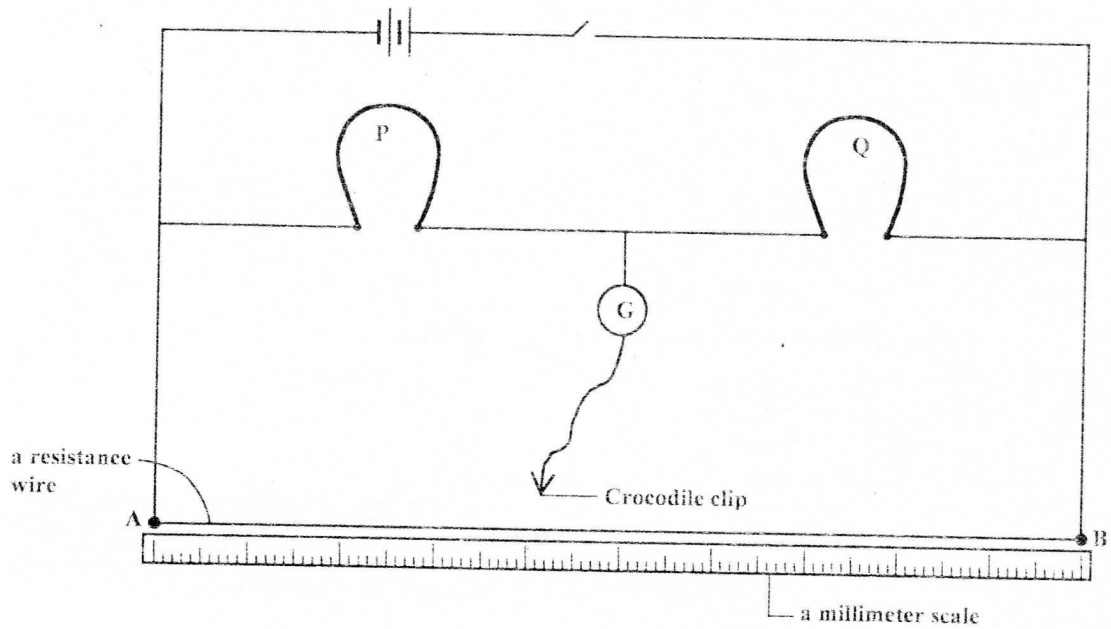


Figure 1

Close the switch. Using the clip at the free end of the wire from the galvanometer, tap wire **AB** near end **A** and observe the deflection in the galvanometer.

- (ii) Then tap the wire near end **B** and again observe the deflection in the galvanometer.
- (iii) Now tap the wire **AB** at various points between **A** and **B** to obtain a point **K** where there is no deflection in the galvanometer.

- (I) Determine the length L_1 , the distance from **A** to **K**.

$L_1 =$ _____ (1 mark)

- (II) Determine the length L_2 , the distance from **B** to **K**.

$L_2 =$ _____ (1 mark)

- (d) (i) Given that the resistance R_Q of Q is 9.0 ohms, determine the resistance R_P of P using the expression:

$$\frac{R_P}{R_Q} = \frac{L_1}{L_2} \quad (2 \text{ marks})$$

.....

.....

.....

- (ii) Determine the value of C_2 given that,

$$C_2 = \sqrt{\frac{R_Q}{R_P}} \quad (2 \text{ marks})$$

.....

.....

.....

- (iii) Compare the value of C_1 (in part (b)) with that of C_2 . (1 mark)

.....

.....

.....

PART B

(e) Set up the circuit shown in **Figure 2**. S and T are crocodile clips.

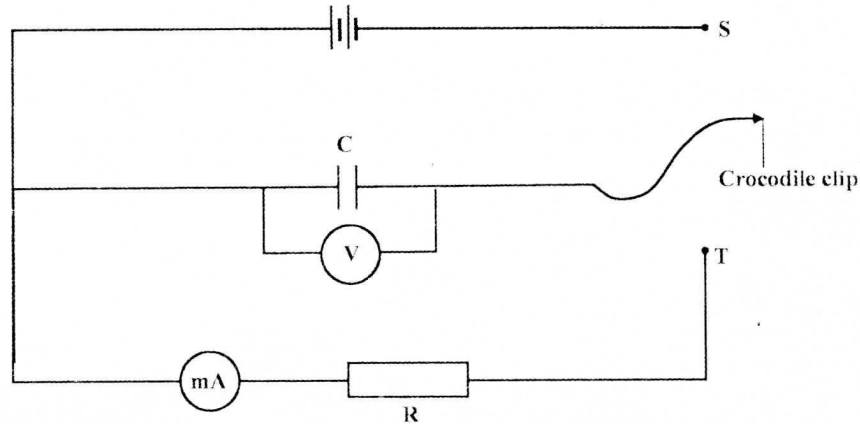


Figure 2

(i) Charge the capacitor **C** by connecting the crocodile clip to **S**. Record the reading of the voltmeter, **V**.

V = _____ (1 mark)

(ii) Calculate the value of the current I_o , given that $I_o = \frac{V}{R}$ (where $R = 4.7 \times 10^3 \Omega$) (3 marks)

.....

.....

.....

(f) (i) Discharge the capacitor by disconnecting the crocodile clip from **S** and connecting it to **T**. Observe and record the highest reading of the milliammeter I_1 . (This is the current at $t_o = 0$). (You may have to repeat the process to obtain an accurate value).

I_1 = _____ (1 mark)

(ii) Recharge the capacitor by connecting the crocodile clip to **S**.

(iii) Discharge the capacitor and at the same time start the stop watch to measure the time t_1 taken for the current to decrease to half the value of I_1 i.e. $\left(\frac{1}{2} I_1\right)$.

t_1 = _____ (1 mark)


- (g) (i) Recharge the capacitor and repeat the procedure in f(iii) to measure the time t_2 taken for the current to decrease to one tenth of the value of I_1 i.e. $(\frac{1}{10}I_1)$.

$t_2 =$ _____

(1 mark)

- (ii) Use the values of the currents $I_1, \frac{1}{2}I_1, \frac{1}{10}I_1$ and their corresponding times to draw a graph of current I (y axis) against time on the grid provided.

(3 marks)

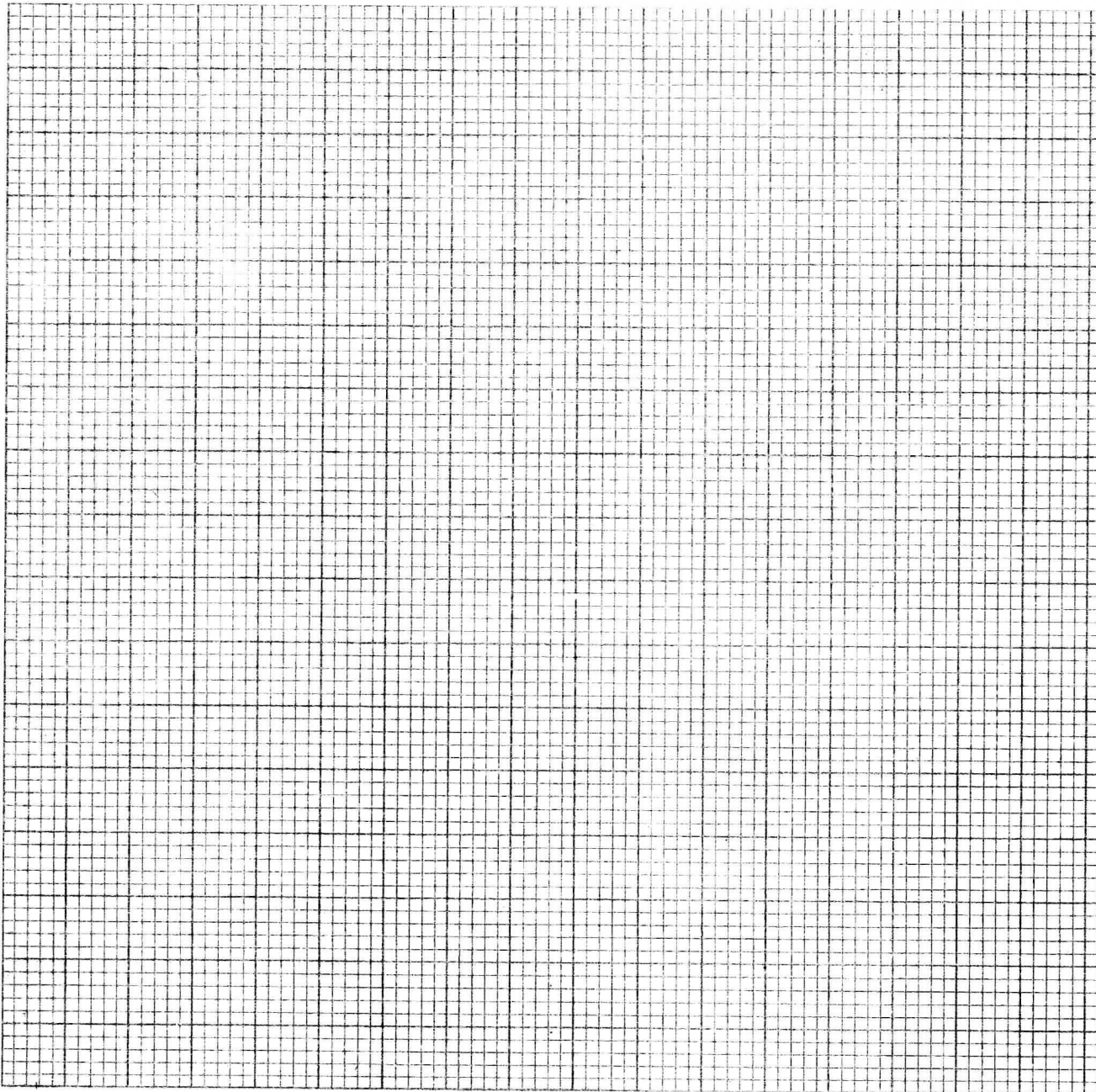

Question 2

You are provided with the following:

- a stand boss and clamp
- two wooden blocks
- a stopwatch
- a half metre rule or metre rule
- a mettalic rod
- a bare copper wire labelled **M** attached to a crocodile clip
- a bare copper wire labelled **N** attached to a crocodile clip.

Proceed as follows:

- (a) Clamp wire **M** between the wooden blocks so that the length l of wire between the wooden blocks and the point of its attachment on the crocodile clip is 5 cm. Clamp the mettalic rod at its mid point using the crocodile clip attached to wire **M**.
(See figure 3)

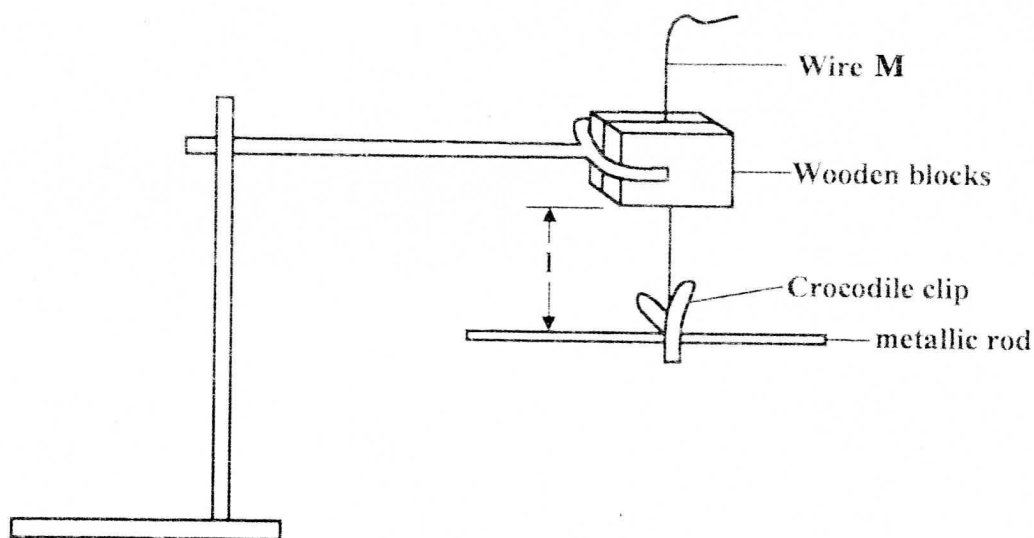


Figure 3

- (b) Displace the rod through a small angle in a horizontal plane about its mid point so that when released, it oscillates in the same plane. Record the time t for 10 oscillations and determine the period **T** in **Table 1**.
- (c) Repeat part (b) for the other lengths of wire **M** shown in **Table 1**.

(d) Complete **Table 1**.


(6 marks)

Table 1

l (cm)	5	10	15	20	25	30
t (s)						
T (s)						
T^2 (s ²)						

(e) Plot a graph of l (y axis) against T^2 .

(5 marks)

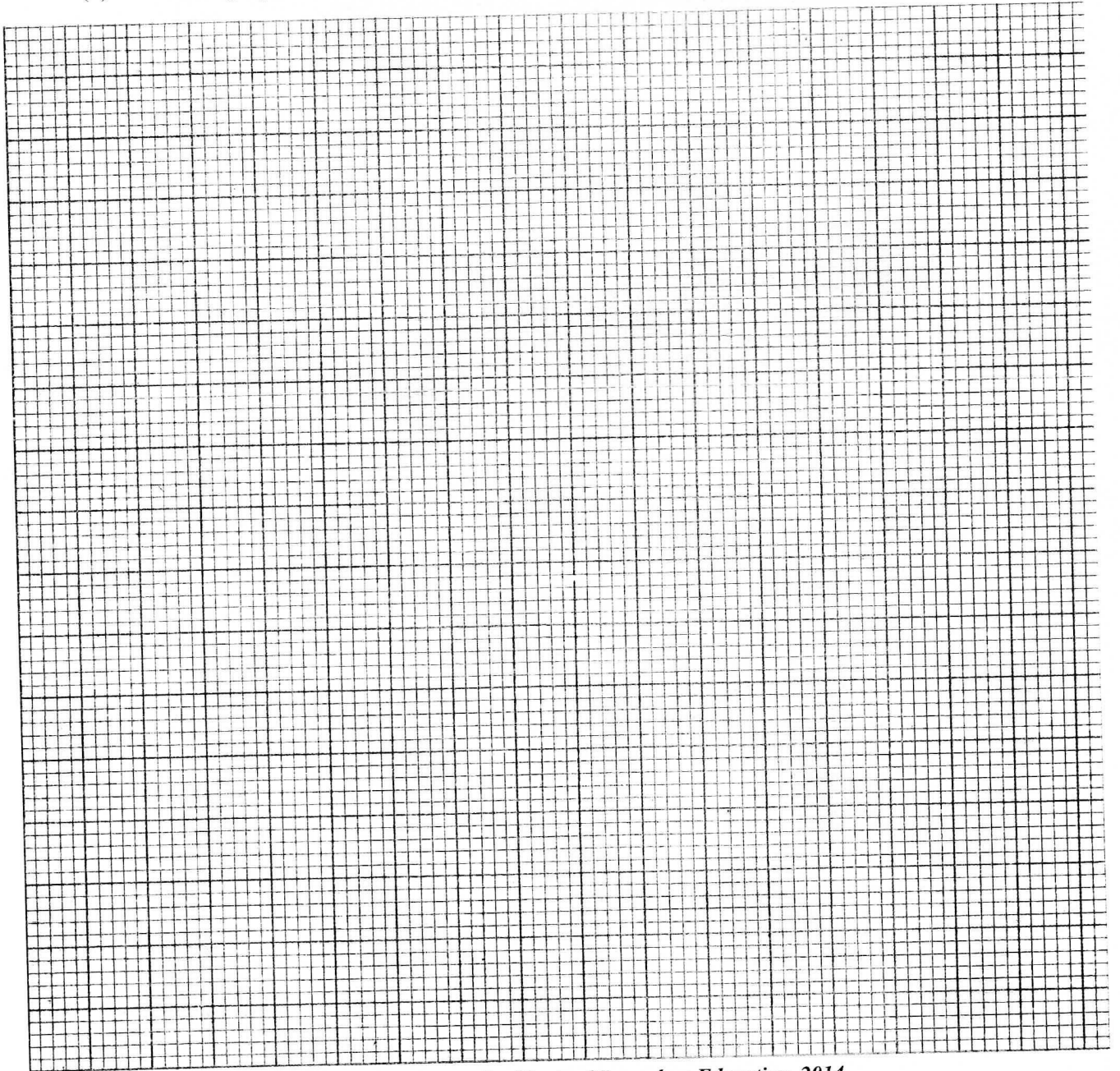

(f) Determine the gradient of the graph, S. (3 marks)

.....
.....
.....

(g) Now replace wire **M** with wire **N** in the set up.

(i) For $l = 20$ cm, displace the rod through a small angle in a horizontal plane and measure the time t_N for 10 oscillations.

$t_N =$ _____ (1 mark)

(ii) Determine the period $T_N =$ _____ (1 mark)

(iii) Calculate T_N^2 (1 mark)

.....
.....
.....

(iv) Determine the value of H given that $H = \frac{0.2}{T_N^2}$. (1 mark)

.....
.....
.....

(v) Calculate the value of $\frac{H}{S}$. (2 marks)

.....
.....

THIS IS THE LAST PRINTED PAGE.